

**Laboratory Assignment 2: Transistors as Switches**  
**ECE 0201: Digital Circuits and Systems**  
**45 Points**

**Name**


张鹤扬 Stafen 0349 & 谢君泽 Gabriel 0374
------------------------------------

**Submission Checklist:**

- ☐ Write within boxes, do not move boxes
- ☐ Write your full name in the box above
- ☐ Save this file as a PDF before uploading, keep the number of pages (**13**) unchanged
- ☐ Note “TO BE CONTINUED” in the answer box if you used the extra pages (11-13)

## Part I: Building a General Logic Source (1 point)

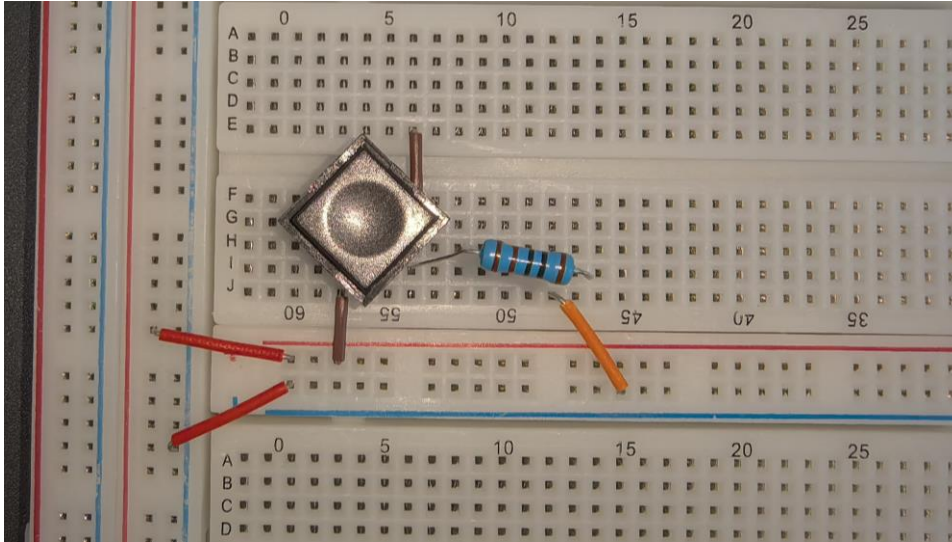[(A) Insert a picture of your build of the circuit in Figure 1] (0.5 points)




[(B) Fill out the following information] (0.5 point)

$V_x$  when the switch is closed = 4.9978V

$V_x$  when the switch is opened = -0.038mV

## Part II: The NMOS Inverter (9 points)

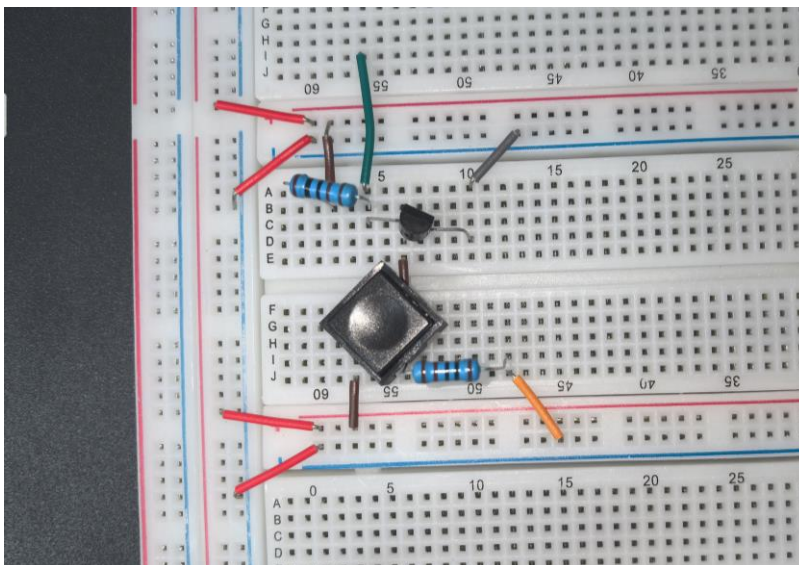[(A) Insert a picture of your build of the circuit in Figure 6] (0.5 points)



[(B) Fill out the following information] (1.0 points)

S1	V <sub>in</sub>	V <sub>out</sub>	LED (on/off)
Open	-0.013mV	4.9753V	ON
Closed	4.9842V	8.042mV	OFF

[(C) Select a logic abstraction and draw a truth table for logical values (0/1)] (2 points)

Logic abstraction: NOT gate

S1	Result
0	1
1	0

Note:

for S1, open is 0, close is 1

for result(LED), ON is 1, OFF is 0

The result is **opposed** to the input, which can be regarded as **NOT gate**.

### NMOS Inverter with R1 = 10kΩ (5.5 points)

[(A) Fill out the following information] (1.0 points)

S1	V <sub>in</sub>	V <sub>out</sub>	LED (on/off)
Open	-0.007mV	4.9708V	ON
Closed	4.9978V	0.921mV	OFF

[(B) Select a logic abstraction and draw a truth table for logical values (0/1)] (2 points)

Logic abstraction: NOT gate

S1	Result
0	1
1	0

Note:

for S1, open is 0, close is 1

for result(LED), ON is 1, OFF is 0

The result is **opposed** to the input, which can be regarded as **NOT gate**.

[(C) Compare  $V_{in}$  and  $V_{out}$  measurements to  $V_{DD}$  and GND. Explain, in terms of known circuit laws, the values you obtained.] (1.5 points)

When  $V_{in}$  is **big enough**, there is **enough voltage differences between G and S** of the NMOS, the NMOS will operate as if it were a **closed switch**, so the  $V_{out}$  is **small**, the **LED is off**.

When  $V_{in}$  is **small**, there is **not enough voltage differences**, the NMOS will act as an **open switch**, so the  $V_{out}$  is **large**, the **LED is on**.


[(D) Explain why the measured voltage ( $V_{out}$ ) changes with resistance.] (1 point)

When the **MOSFET is OFF**, the resistor (R) and voltmeter are connected in series. Since the **voltmeter has a constant internal resistance and the resistor's resistance increases**, an increase in R will result in a **larger voltage drop** across R, leaving a smaller voltage for the voltmeter to measure.

When **the MOSFET is ON**, a larger R **reduces the current** flowing through the circuit. Consequently, the voltmeter will detect a **smaller voltage drop**, reflecting the diminished current.

### Part III: The NMOS NAND Gate (9.5 points)

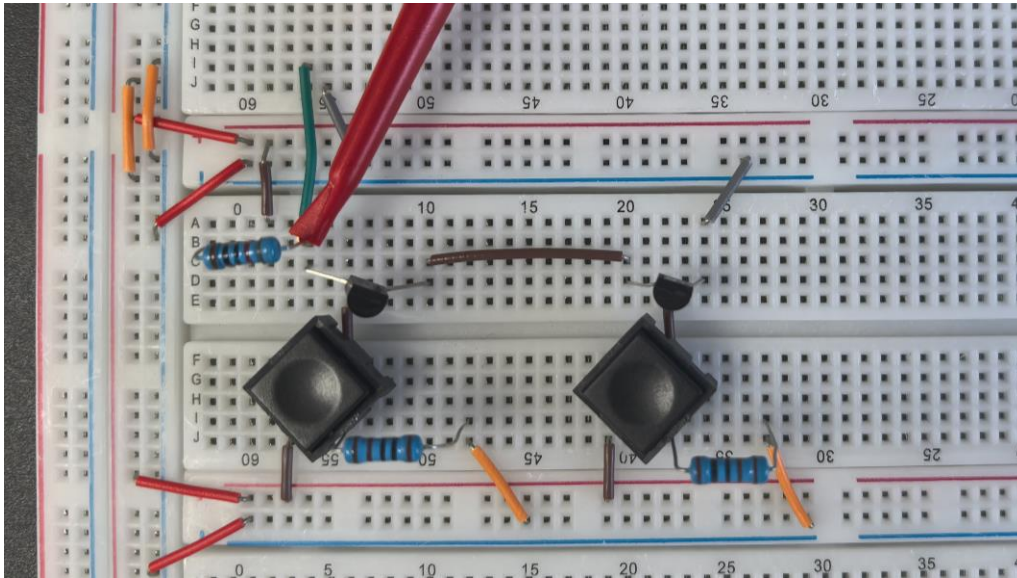[(A) Insert a picture of your build of the circuit] (0.5 points)



[(B) Fill out the following information] (2 points)

S1 (A)	S2 (B)	V <sub>out</sub>	LED (on/off)
Open	Open	4.9753V	ON
Open	Closed	4.9748V	ON
Closed	Open	4.9752V	ON
Closed	Closed	15.000mV	OFF

[(C) Select a logic abstraction and draw a truth table for logical values (0/1)] (2 points)

Logic abstraction: NAND gate

S1	S2	Result
0	0	1
0	1	1
1	0	1
1	1	0

Note:

for switches (S1,S2), open is 0, close is 1

for result(LED), ON is 1, OFF is 0

The result is 0 **if and only** if two inputs are **both** 1, which can be regarded as **NAND gate**.

### NMOS NAND Gate with $R1 = 10k\Omega$ (5 points)

[(A) Fill out the following information] (2 points)

S1 (A)	S2 (B)	$V_{out}$	LED (on/off)
Open	Open	4.9708V	ON
Open	Closed	4.9703V	ON
Closed	Open	4.9703V	ON
Closed	Closed	1.781mV	OFF

[(B) Select a logic abstraction and draw a truth table for logical values (0/1)] (2 points)

Logic abstraction: NAND gate

S1	S2	Result
0	0	1
0	1	1
1	0	1
1	1	0

Note:

for switches (S1,S2), open is 0, close is 1

for result(LED), ON is 1, OFF is 0

The result is 0 **if and only** if two inputs are **both** 1, which can be regarded as **NAND gate**.

[(C) Which resistor value works better in this circuit in terms of the circuit's logic output (High/Low)? Why?] (1 point)

The **smaller resistor value ( $1k\Omega$ )** works better than the larger one for  $R1$  in this NAND gate circuit.


The **smaller  $R1$  ( $10k\Omega$ )** provides **stronger pull-up capability** when the MOSFETs are off, which **ensures the output ( $V_{out}$ ) is pulled firmly to the High level** even when driving light loads, minimizing voltage drops caused by loads.

The **larger  $R1$  ( $10k\Omega$ )** weakens the pull-up ability, making  $V_{out}$  **more susceptible to voltage drops** under load, which could **blur the distinction** between High and Low levels.

[(D) Demonstrate your circuit to the TA for the first Lab 2 check-off .] (7 points)

## Part IV: The CMOS Inverter (5.5 points)

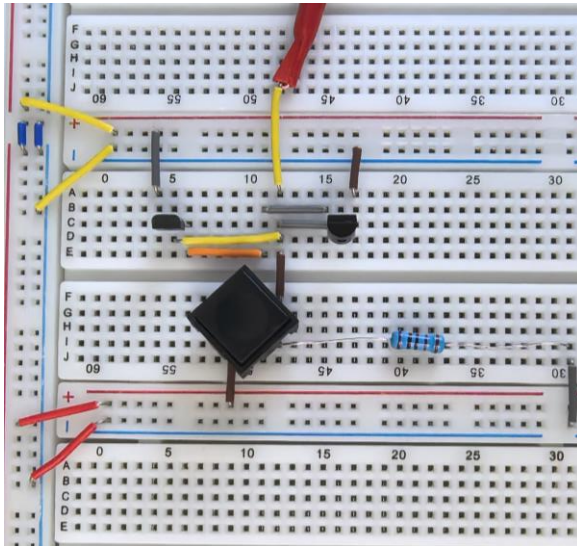[(A) Insert a picture of your build of the circuit] (0.5 points)



[(B) Fill out the following information] (1.0 points)

S1	$V_A$	$V_{out}$	LED (on/off)
Open	-0.036mV	4.9758V	ON
Closed	4.9979V	19.436mV	OFF

[(C) Select a logic abstraction and draw a truth table for logical values (0/1)] (2 points)

Logic abstraction: NOT gate

S1	Result
0	1
1	0

Note:

for S1, open is 0, close is 1

for result(LED), ON is 1, OFF is 0

The result is **opposed** to the input, which can be regarded as **NOT gate**.

[(D) How does one switch control 2 transistors? Under what conditions are both transistors turned on? Why?] (2 points)

Both transistors share the same control signal because **their gates(G) are connected together** and driven by the same voltage  $V_A$ .

When  $V_A = 0V$ , the PMOS has a negative gate-to-source voltage and **turns on**, while the NMOS has zero gate-to-source voltage and **remains off**. When  $V_A = 5V$ , the **PMOS turns off** and the **NMOS turns on**.


When  $V_A$  is at a mid-level voltage, **both transistors meet their conduction conditions** and are **on** simultaneously.

This happens because the PMOS conducts when **its gate is lower than its source**, and the NMOS conducts when **its gate is higher than its source**.



## Part V: The CMOS NAND Gate (20 points)

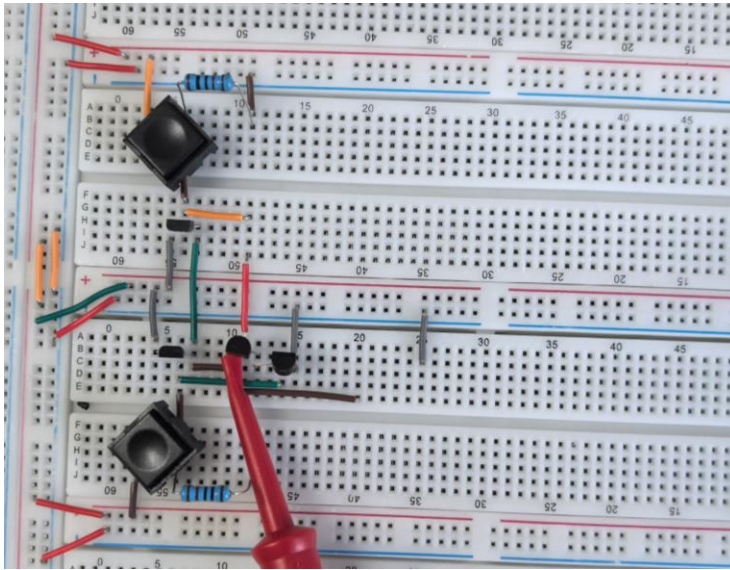[(A) Insert a picture of your build of the circuit] (0.5 points)



[(B) Fill out the following information] (2 points)

S1 (A)	S2 (B)	V <sub>A</sub>	V <sub>B</sub>	V <sub>out</sub>	LED (on/off)
Open	Open	0.014mV	0.991V	4.9080V	ON
Open	Closed	0.063mV	4.998V	4.998V	ON
Closed	Open	4.909V	0.728V	4.907V	ON
Closed	Closed	4.905V	4.919V	0.991mV	OFF

[(C) Select a logic abstraction and draw a truth table for logical values (0/1)] (2 points)

Logic abstraction: NAND gate

S1	S2	Result
0	0	1
0	1	1
1	0	1
1	1	0

Note:

for switches (S1,S2), open is 0, close is 1

for result(LED), ON is 1, OFF is 0

The result is 0 **if and only** if two inputs are **both** 1, which can be regarded as **NAND gate**.

[(D) What is the difference between an NMOS NAND gate and a CMOS NAND gate?] (1.5 points)

An **NMOS NAND gate** uses only NMOS transistors with pull-up resistors, so it **consumes power when it stand-by** and **cannot** drive a full logic high.

A **CMOS NAND gate** uses both PMOS and NMOS transistors in **complementary pairs**, so it **can** drive a full logic high, and very **low static power consumption**.

[(E) Demonstrate your circuit to the TA for the second Lab 2 check-off.] (7 points)

## EXTRA PAGES

[Leave the page unchanged if you are not going to use. Otherwise, specify the problem number you are working on here. Don't forget to notify "TO BE CONTINUED" in the original problem box]

## EXTRA PAGES

[Leave the page unchanged if you are not going to use. Otherwise, specify the problem number you are working on here. Don't forget to notify "TO BE CONTINUED" in the original problem box]

## EXTRA PAGES

[Leave the page unchanged if you are not going to use. Otherwise, specify the problem number you are working on here. Don't forget to notify "TO BE CONTINUED" in the original problem box]